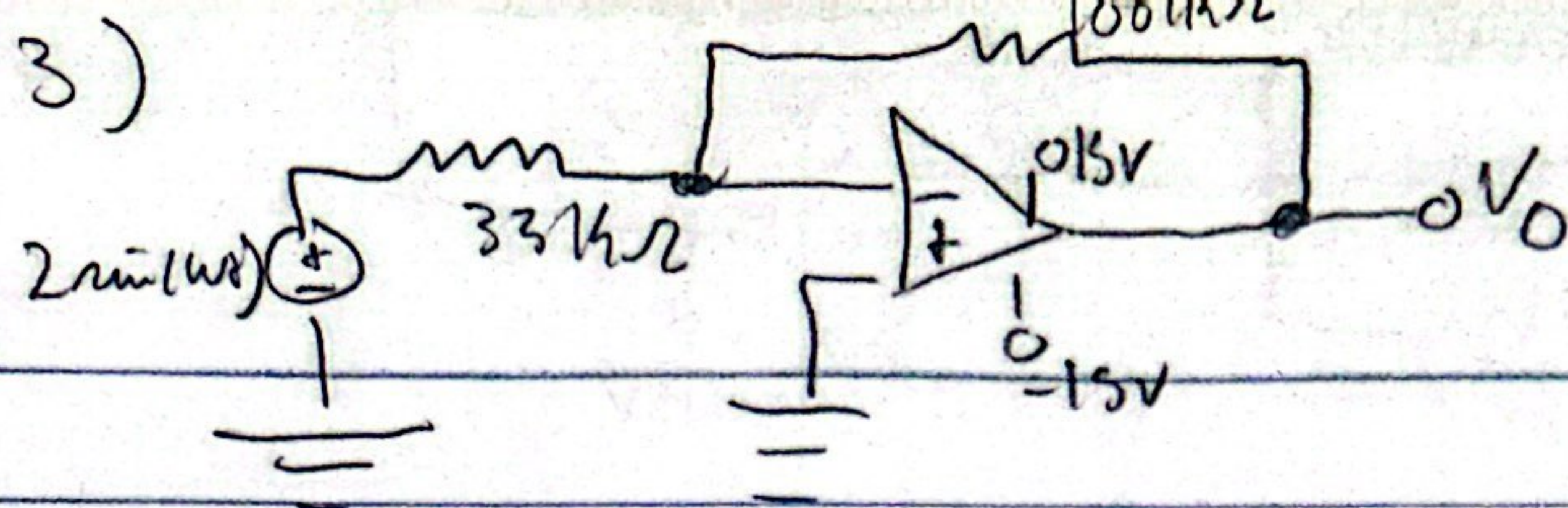


circuits
part
2

3)



$$b_n \geq 2\pi f_{FP} \cdot V_{p1n} \text{ so, } f_{FP} = \frac{b_n}{2\pi V_{p1n}}$$

$$GBW = A_{CL} \cdot f_{CL} \text{ so, } f_{CL} = \frac{GBW}{A_{CL}}$$

$$A_{CL} = \frac{R_f}{R_{in}} = \frac{100k\Omega}{33k\Omega} = \boxed{3.03}$$

$$f_{FP} = \frac{0.5e^6}{2\pi \cdot 6} \approx \frac{500,000}{37.7} = 13,250 \text{ Hz} \approx \boxed{13.25 \text{ kHz}}$$

$$f_{CL} = \frac{GBW}{A_{CL}} = \frac{1,000,000}{3.03} \approx 330,000 \text{ Hz} = \boxed{330 \text{ kHz}}$$