

Homework - Study Problems Chapter 2

From the textbook “Electric Circuits” by Nilsson and Riedel (11th edition), work the following problems:

- 2.1 answer: 1700 W
- 2.2 answer: a) Valid
 b) 18 V absorbing, 7 V absorbing, 5 mA delivering
 c) 125 mW
 d) ? optional practice
- 2.3 answer: Invalid interconnection
- 2.4 answer: 300 W
- 2.7 answer: a) 20 V
 b) 8 W absorbed
- 2.8 answer: Invalid interconnection
- 2.9 answer: 210 W
- 2.17 answer: a) 1.2 A, 0.3 A
 b) 120 V
 c) 180 W
- 2.20 answer: a) 25 V
 b) 575 mW delivered, same absorbed
- 2.21 answer: a) 0.02 A
 b) 7.5 V
 c) 10 V
 d) 0.5 W
- 2.25 answer: a) -9 A
 b) $P_{9\Omega}$: 36 W, $P_{11\Omega}$: 44 W, $P_{10\Omega}$: 40 W, $P_{5\Omega}$: 180 W, $P_{30\Omega}$: 270 W,
 $P_{4\Omega}$: 100 W, $P_{16\Omega}$: 400 W, $P_{15\Omega}$: 240 W
 c) 190 V
 d) 1710 W
- 2.26 answer: a) 1.6 Ω
 b) 6960 W
- 2.27 answer: 2 k Ω

(Note: power developed is the same as total power delivered)