

ECE212 Exam Formula Sheet


① Basic Techniques / Fundamentals

1. Voltage and Current Division:

$$V_x = \frac{R_x}{R_{\text{eq}}} V_s$$


$$I_x = \frac{R_{\text{eq}}}{R_x + R_{\text{eq}}} I_s$$

2. Source Transformation

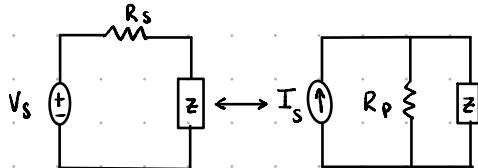

$$V_s = I_s R_p \text{ and } R_s = R_p$$

3. Thevenin and Norton

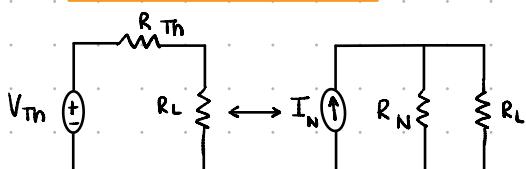

$$V_{\text{th}} = V_{\text{oc}} = I_N R_{\text{th}}$$

$$R_n = R_{\text{th}} = \frac{V_{\text{th}}}{I_{\text{sc}}}$$

$$I_{\text{sc}} = I_N$$

$$\rightarrow \text{Max Power: } R_L = R_{\text{th}}$$

$$P_{\text{max}} = \frac{(V_{\text{th}})^2}{4R_{\text{th}}}$$

4. Power / Capacitor / Inductor

$$P = VI = \frac{V^2}{R} = I^2 R$$

• **Capacitor** → goes to open circuit

$$I_C(t) = C \frac{dV_C(t)}{dt}$$

→ in parallel: $C_{\text{eq}} = C_1 + C_2 + \dots$

→ in series: $\frac{1}{C_{\text{eq}}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots$

• **Inductor** → goes to short circuit

$$V_L(t) = L \frac{di(t)}{dt}$$


→ in parallel: $\frac{1}{L_{\text{eq}}} = \frac{1}{L_1} + \frac{1}{L_2} + \dots$

→ in series: $L_{\text{eq}} = L_1 + L_2 + \dots$

② Operational Amplifier


- ideal op amp → 0 input current → $V_P = V_N$ infinite gain

1. Non-Inverting

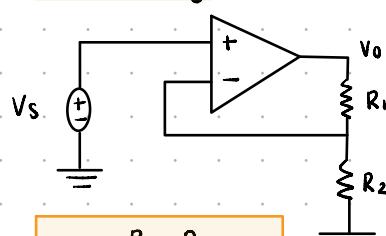

$$V_o = \frac{R_1 + R_2}{R_2} V_s$$


2. Voltage follower / Buffer

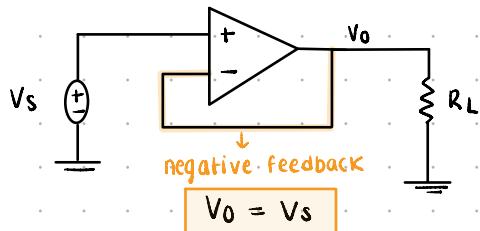

negative feedback


$$V_o = V_s$$

3. Inverting Amplifier

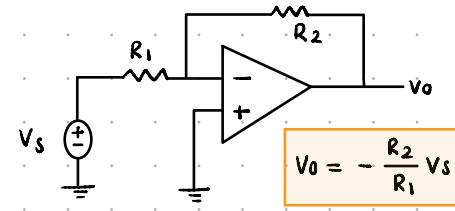


$$V_o = -\frac{R_2}{R_1} V_s$$

4. Summing Amplifier

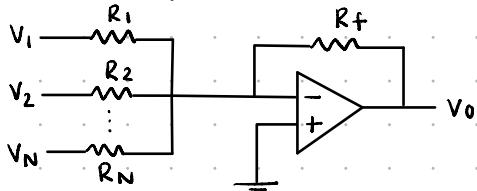

$$V_o = -R_f \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} + \dots + \frac{V_N}{R_N} \right)$$

5. Differential Amplifier

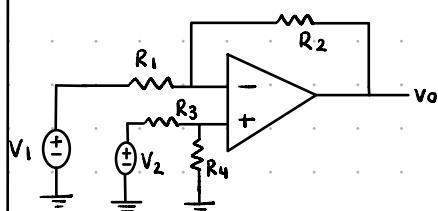


$$V_o = -\frac{R_2}{R_1} V_1 + \frac{R_4}{R_3 + R_4} \frac{R_1 + R_2}{R_1} V_2$$

$$\rightarrow \text{when } \frac{R_3}{R_1} = \frac{R_4}{R_2}$$


$$V_o = \frac{R_2}{R_1} (V_2 - V_1)$$

6. Inverting Integrator

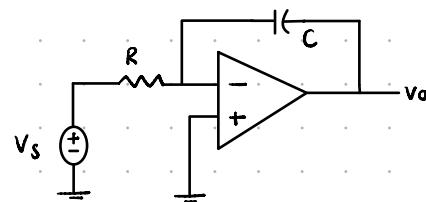

$$V_o(t) = V_o(t_0) - \frac{1}{RC} \int V_s(t) dt$$



7. Integrating Differentiator

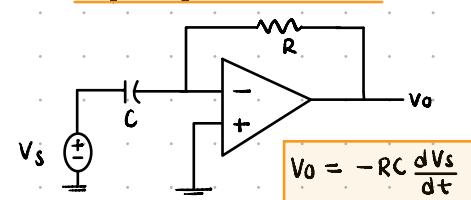

$$V_o = -RC \frac{dV_s}{dt}$$

③ 1st and 2nd Order Circuits

1. First Order: RC and RL Circuits

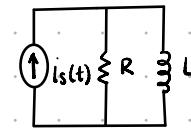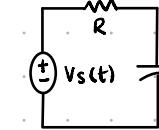

$$RC: \frac{dV(t)}{dt} + \frac{1}{RC} V(t) = \frac{1}{RC} V_s(t)$$

$$RL: \frac{dI(t)}{dt} + \frac{R}{L} I(t) = \frac{R}{L} I_s(t)$$

2. First order: Step Response

$$RC: V_c(t) = V_c(\infty) + e^{-t/\tau} [V_c(0) - V_c(\infty)]$$

$$RL: i_L(t) = i_L(\infty) + e^{-t/\tau} [i_L(0) - i_L(\infty)]$$

where $\tau = R_{\text{th}} C$ or $\tau = \frac{L}{R_{\text{th}}}$

3. Second Order: Series RLC circuit capacitor voltage:

$$V_c'' + \frac{R}{L} V_c' + \frac{1}{LC} V_c = \frac{V_s}{LC}$$

Inductor current:

$$i_L'' + \frac{R}{L} i_L' + \frac{1}{LC} i_L = 0$$

4. Second Order: Parallel RLC circuit capacitor voltage

$$V_c'' + \frac{1}{RC} V_c' + \frac{1}{LC} V_c = 0$$

Inductor current:

$$i_L'' + \frac{1}{RC} i_L' + \frac{1}{LC} i_L = \frac{i_s}{LC}$$

5. Second Order: Steps to solve

1. find initial and final conditions

steady state

$x(\infty), x(0), x'(0)$

capacitor: $V_c(0+) = V_c(0^-)$

$$i_c(0) = C \frac{dV_c(0)}{dt}$$

inductor: $i_L(0+) = i_L(0^-)$

$$V_L(0) L \frac{di_L(0)}{dt}$$

2. find form of transient response

→ zero all independent sources

→ solve characteristic eqn.

i) overdamped (two roots):

$$x(t) = x(\infty) + K_1 e^{s_1 t} + K_2 e^{s_2 t}$$

ii) critically damped (one root):

$$x(t) = x(\infty) + K_1 e^{s_1 t} + K_2 t e^{s_1 t}$$

iii) underdamped (complex roots):

$$x(t) = x(\infty) + e^{xt} (K_1 \cos \omega t + K_2 \sin \omega t)$$

3. write eqn. and solve for coeff.

④ AC Circuit Analysis

1. Phasors: phasor representation of a sinusoid $v(t) = V_A \cos(\omega t + \phi)$

$$\bar{V} = V_A e^{j\phi} = V_A / \phi$$

$$= V_A \cos\phi + j V_A \sin\phi$$

2. Phasor Circuit Analysis

• Impedances (phasor domain) [Ω]

$$Z_R = R$$


$$Z_L = j\omega L$$

$$Z_C = \frac{1}{j\omega C} = \frac{-j}{\omega C}$$

→ use same techniques (i.e. superposition, Thevenin, etc.) to solve circuit

→ convert back to time domain (if needed)

3. Effects of ω on Impedance

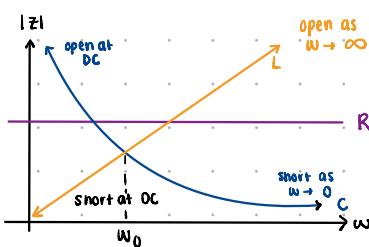

⑤ Mutual Inductance


inductor 1 and inductor 2:

$$V_1(t) = L_1 \frac{di_1}{dt} \pm M \frac{di_2}{dt}$$

$$V_2(t) = L_2 \frac{di_2}{dt} \pm M \frac{di_1}{dt}$$

Dot convention (to determine sign of second term):

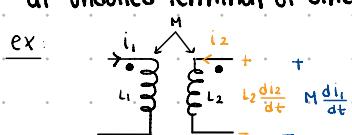- i) current entering dotted terminal → positive voltage at dotted terminal of other coil
- ii) current entering undotted terminal → positive voltage at undotted terminal of other coil



Coupling coefficient

$$K = \frac{M}{\sqrt{L_1 L_2}} \leq 1$$

→ $K=1$ is perfect coupling

⑥ Transformers

$$\text{eq. 1: } \frac{V_2(t)}{V_1(t)} = \pm \frac{N_2}{N_1} = \pm n$$

$$\text{eq. 2: } \frac{i_2(t)}{i_1(t)} = \pm \frac{1}{n}$$

→ $n > 1$: step up transformer


→ $n < 1$: step down transformer

to determine sign:

i) if V_1 and V_2 are both +ve or -ve at dotted terminal use +n for eq. 1 (otherwise -n)


ii) if i_1 and i_2 both enter into or leave the dotted terminal, use -n for eq. 2 (otherwise +n)

(1) $N_1 : N_2$

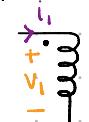


$$\frac{V_2}{V_1} = n, \frac{i_2}{i_1} = \frac{1}{n}$$

(2) $N_1 : N_2$

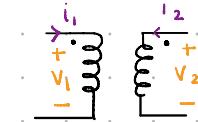


$$\frac{V_2}{V_1} = n, \frac{i_2}{i_1} = -\frac{1}{n}$$

(3) $N_1 : N_2$

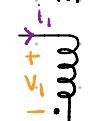

$$\frac{V_2}{V_1} = -n, \frac{i_2}{i_1} = \frac{1}{n}$$

(4) $N_1 : N_2$

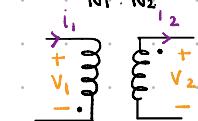

$$\frac{V_2}{V_1} = -n, \frac{i_2}{i_1} = -\frac{1}{n}$$

• reflected impedance

$$Z_{in} = \frac{Z_L}{n^2} \rightarrow \text{equivalent impedance on secondary side}$$

⑦ Complex Power

1. Instantaneous power

$$p(t) = v(t)i(t)$$

$$= V_A \cos(\omega t + \theta_v) I_A \cos(\omega t + \theta_i)$$

(time dependent)

2. Average Power

$$P_{avg} = \frac{V_A I_A}{2} \cos(\theta_v - \theta_i)$$

→ P_{avg} for capacitors and inductors is 0

3. RMS value

$$X_{rms} = \sqrt{\frac{1}{T} \int_0^T x^2 dt}$$

$$V_{rms} = \frac{V_m}{\sqrt{2}} \text{ and } I_{rms} = \frac{I_m}{\sqrt{2}}$$

$$P_{avg} = V_{rms} \cdot I_{rms} \cos(\theta_v - \theta_i)$$

for resistor: $P_{avg} = I_{rms}^2 R = \frac{V_{rms}^2}{R}$

4. Apparent Power and Power factor

$$S = V_{rms} I_{rms}$$

$$pf = \cos(\theta_v - \theta_i) = \frac{P}{S}$$

purely reactive $0 \leq pf \leq 1$ purely resistive
(i.e. capacitors/inductors only)

5. Complex Power


→ complex conjugate

$$S = \bar{V}_{rms} \bar{I}_{rms}^* = V_{rms} I_{rms} / \theta_v - \theta_i$$

$$= I_{rms} Z = \frac{V_{rms}^2}{Z^*} = P + jQ$$

→ where $Z = (R + jX)$

power triangle

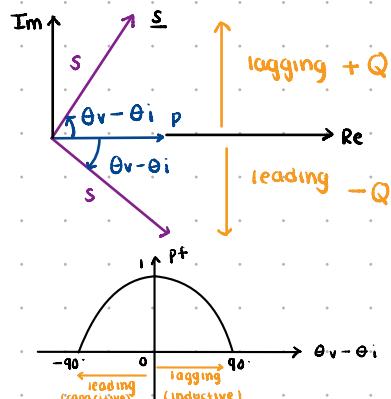


6. Max Power Transfer

$$Z_L = Z_{th}^* = R_{th} - j X_{th}$$

$$P_{max} = \frac{1}{4} \frac{|V_{th} I_{th}|^2}{R_{th}} = \frac{|V_m|^2}{8 R_{th}}$$

⑧ Laplace

• convert to Laplace domain:

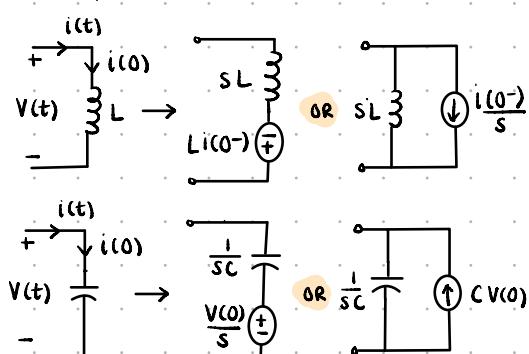

Resistor: $V(s) = R I(s)$

Inductor: $V(s) = sLI(s)$

Capacitor: $V(s) = \frac{1}{sC} I(s)$

$\rightarrow Z \{u(t)\} = \frac{1}{s}$

• Use regular techniques to solve, Z^{-1} to switch back to time domain

9 Transfer Function and Bode Plots

1 Types of Transfer Functions

voltage gain: $H(w) = \frac{V_o(w)}{V_i(w)}$

current gain: $H(w) = \frac{I_o(w)}{I_i(w)}$

transfer impedance: $H(w) = \frac{V_o(w)}{I_i(w)}$

transfer admittance: $H(w) = \frac{I_o(w)}{V_i(w)}$

2 Steps to Draw Bode Plot given $H(jw)$

i) Write $H(jw)$ in standard form,

→ i.e. all terms in the form

$$\left(\frac{jw}{x} + 1 \right)$$

ii) determine break frequencies

iii) write the magnitude and phase equations using components of the equation

iv) plot for different values of w

3 Types of Filters

ex

$$H(w) = \frac{200jw}{(jw+2)(jw+10)}$$

ii) $H(w) = \frac{10jw}{\left(\frac{jw}{2} + 1\right)\left(\frac{jw}{10} + 1\right)}$

iii) $w = 2$ and $w = 10$ are break frequencies

$$H_{dB} = 20 \log(10) + 20 \log |jw| - 20 \log \left| 1 + \frac{jw}{2} \right| - 20 \log \left| 1 + \frac{jw}{10} \right|$$

$$\Phi = 90 - \tan^{-1} \frac{w}{2} - \tan^{-1} \frac{w}{10}$$

$H(dB)$

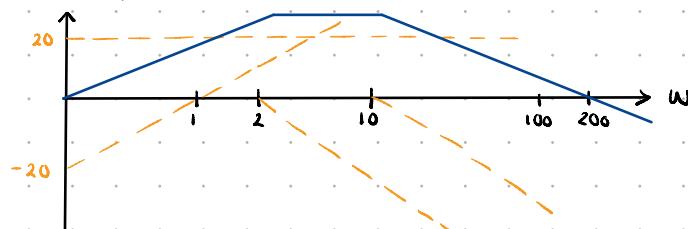


TABLE 14.5

Summary of the characteristics of ideal filters.

Type of Filter	$H(0)$	$H(\infty)$	$H(\omega_c)$ or $H(\omega_0)$
Low-pass	1	0	$1/\sqrt{2}$
High-pass	0	1	$1/\sqrt{2}$
Band-pass	0	0	1
Band-stop	1	1	0

ω_c is the cutoff frequency for low-pass and high-pass filters; ω_0 is the center frequency for band-pass and band-stop filters.

TABLE 14.3

Summary of Bode straight-line magnitude and phase plots.












Factor	Magnitude	Phase
K	$20 \log_{10} K$	
$(j\omega)^N$		
$\frac{1}{(j\omega)^N}$		
$\left(\frac{1+j\omega}{z}\right)^N$		
$\frac{1}{(1+j\omega/p)^N}$		
$\left[1 + \frac{2j\omega\xi}{\omega_n} + \left(\frac{j\omega}{\omega_n}\right)^2\right]^N$		
$\frac{1}{[1 + 2j\omega\xi/\omega_k + (j\omega/\omega_k)^2]^N}$		

Table of Laplace Transforms

$f(t)$	$F(s)$	$f(t)$	$F(s)$
$u(t)$	$\frac{1}{s}$	$\cos kt$	$\frac{s}{s^2 + k^2}$
t	$\frac{1}{s^2}$	$\sin kt$	$\frac{k}{s^2 + k^2}$
t^2	$\frac{2!}{s^3}$	$\cosh kt$	$\frac{s}{s^2 - k^2}$
t^n	$\frac{n!}{s^{n+1}}$	$\sinh kt$	$\frac{k}{s^2 - k^2}$
e^{at}	$\frac{1}{s - a}$	$e^{at} \cos kt$	$\frac{s - a}{(s - a)^2 + k^2}$
		$e^{at} \sin kt$	$\frac{k}{(s - a)^2 + k^2}$

Table of Properties of the Laplace Transform

$f(t)$	$F(s)$
$\alpha f(t) + \beta g(t)$	$\alpha F(s) + \beta G(s)$
$f^{(n)}(t)$	$s^n F(s) - s^{n-1}f(0) - \dots - f^{(n-1)}(0)$
$\int_0^t f(\tau) d\tau$	$\frac{F(s)}{s}$
$\int_0^t f(\tau)g(t - \tau) d\tau$	$F(s)G(s)$
$t^n f(t)$	$(-1)^n F^{(n)}(s)$
$e^{at} f(t)$	$F(s - a)$
$f(t - a)u(t - a)$	$e^{-as} F(s)$
$f(t)u(t - a)$	$e^{-as} \mathcal{L}\{f(t + a)\}$
$f(t) = f(t + T)$	$\frac{1}{1 - e^{-sT}} \int_0^T e^{-st} f(t) dt$

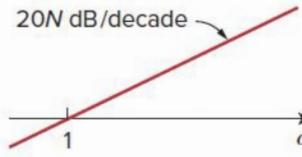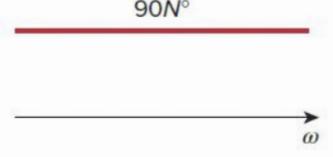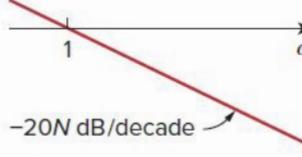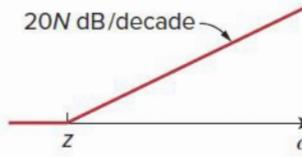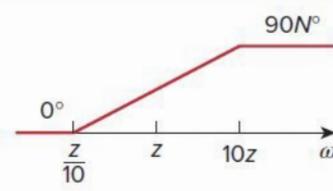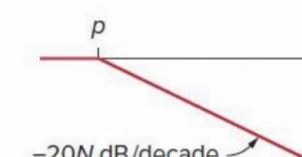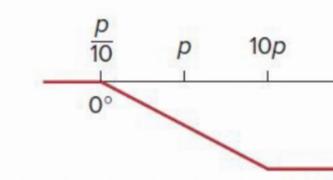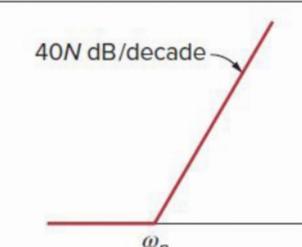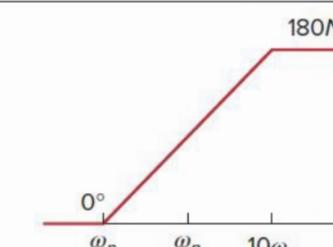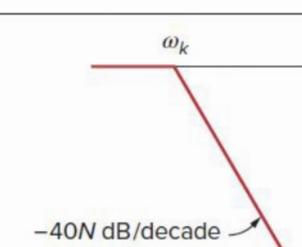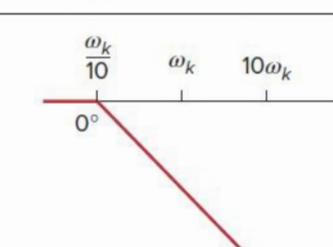