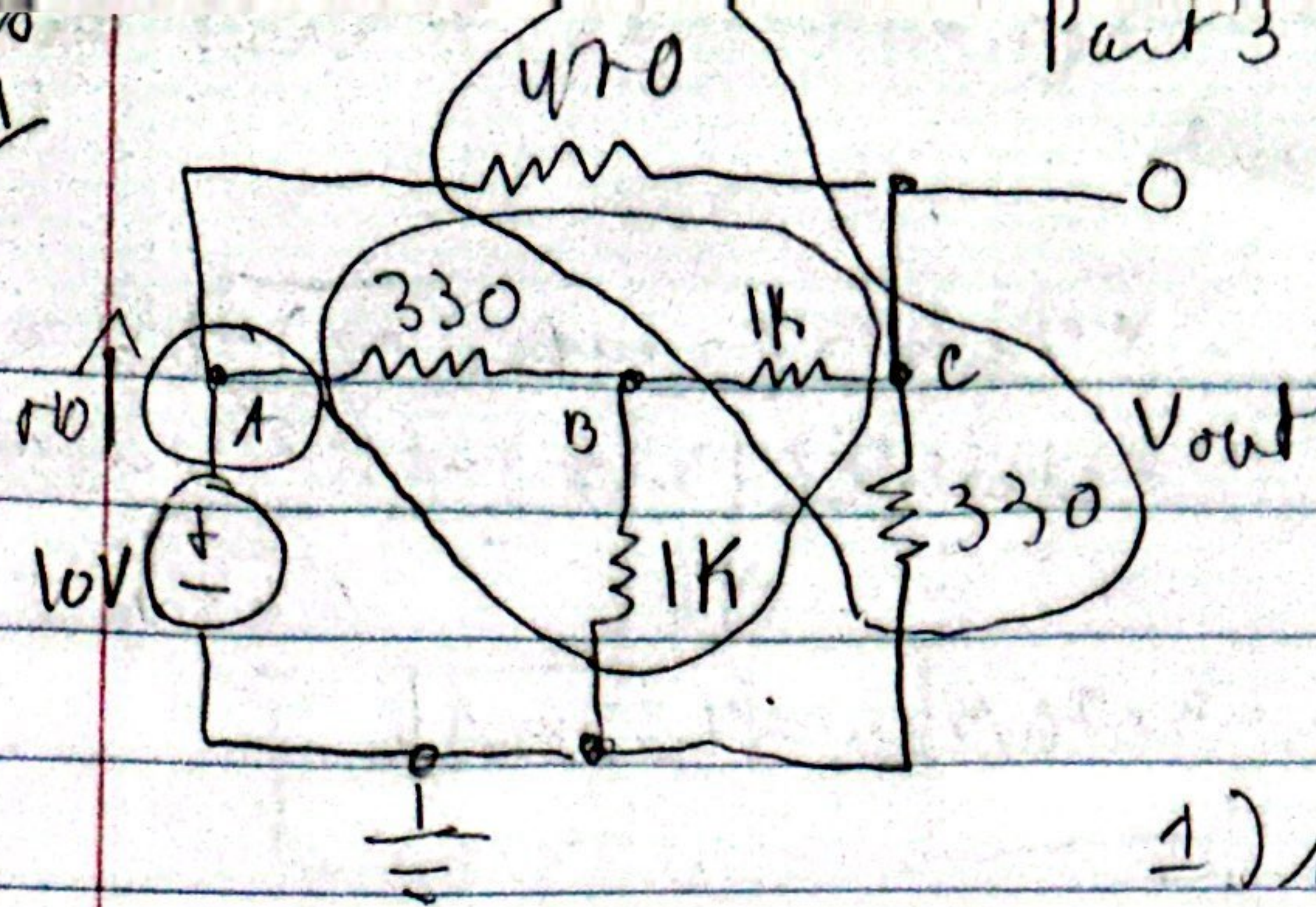


circuits
part 1

Part 3 circuit analysis



node A: top of the 10V source
fixed at $V_A = 10V$

node B: middle junction (330Ω & $1k\Omega$)

node C: right junction (470Ω , $1k\Omega$, 330Ω)

Resistors:

A-B: 330Ω

B-C: $1k\Omega$

A-C: 470Ω

B-ground: $1k\Omega$

C-ground: 330Ω

1) Node voltage analysis $V_B = 6.92V$, $V_C = 4.58V$

Kcl at node B:

$$\frac{V_B - V_A}{330} + \frac{V_B - V_C}{1000} + \frac{V_B - 0}{1000} = 0$$

$V_A = 10V$

ground = $0V$

$$\frac{V_B - 10}{330} + \frac{V_B - V_C}{1000} + \frac{V_B - 0}{1000} = 0$$

$$\frac{1000}{330}(V_B - 10) + (V_B - V_C) + V_B = 0$$

$$(3.0303 + 2)V_B - V_C = 30.30303$$

$$5.0303V_B - V_C = 30.30303$$

2) Kcl at node C:

$$\frac{V_C - V_A}{470} + \frac{V_C - V_B}{1000} + \frac{V_C - 0}{330} = 0$$

$$(\times 1000) \frac{V_C - 10}{470} + \frac{V_C - V_B}{1000} + \frac{V_C}{330} = 0$$

$$\frac{1000}{470}(V_C - 10) + (V_C - V_B) + \frac{1000}{330}V_C = 0$$

$$-V_B + (2.127 + 1 + 3.0303)V_C = 21.2765$$

$$-V_B + 6.157963V_C = 21.276596$$

3) Solving (B) - (C):

$$(C) \quad V_B = 6.1579 \quad V_C = 21.2765$$

put into B

$$5.0303(6.1579V_C - 21.2765) - V_C = 30.3030$$

$$(30.9764 - 1)V_C - 107.02 = 30.3030$$

$$29.976422V_C = 137.32 \quad V_C = 4.58V$$

$$V_B = 6.157(4.58) - 21.27 = 6.92V$$

Circuits
Lab 1

Part 3 analysis

2) currents in every element

$$I = \frac{V_{\text{left}} - V_{\text{right}}}{R}$$

$$\text{* checks B } (2.344 + 6.92) - 9.33 = 0 \checkmark$$

$$\text{* checks C } (13.88) - (11.53 + 2.344) = 0 \checkmark$$

through A-B (330Ω)

$$\Delta V = 10 - 6.92 = 3.076 \text{ V} \rightarrow I_{AB} = 3.076 / 330 = \boxed{9.33 \text{ mA}}$$

through B-C ($1 \text{ k}\Omega$)

$$\Delta V = 6.92 - 4.58 = 2.344 \text{ V} \rightarrow I_{BC} = \boxed{2.344 \text{ mA}}$$

through A-C (470Ω)

$$\Delta V = 10 - 4.58 = 5.421 \text{ V} \rightarrow I_{AC} = 5.421 / 470 = \boxed{11.53 \text{ mA}}$$

$$\text{B to ground } (1 \text{ k}\Omega) I_{B\downarrow} = V_B / 1000 = 6.92 / 1000 = \boxed{6.92 \text{ mA}}$$

$$\text{C to ground } (330 \Omega) I_{C\downarrow} = V_C / 330 = \boxed{13.88 \text{ mA}}$$

3) Power dissipated $P = \frac{(\Delta V)^2}{R}$

$$\bullet 330 \Omega \text{ (A-B)} P_{AB} = (3.076)^2 / 330 = \boxed{28.2 \text{ mW}}$$

$$\bullet 1 \text{ k}\Omega \text{ (B-C)} P_{BC} = (2.344)^2 / 1000 = \boxed{5.50 \text{ mW}}$$

$$\bullet 470 \Omega \text{ (A-C)} P_{AC} = (5.421)^2 / 470 = \boxed{62.6 \text{ mW}}$$

$$\bullet 1 \text{ k}\Omega \text{ (B-G)} P_{B\downarrow} = (6.92)^2 / 1000 = \boxed{47.9 \text{ mW}}$$

$$\bullet 330 \Omega \text{ (C-G)} P_{C\downarrow} = (4.58)^2 / 1000 = \boxed{63.6 \text{ mW}}$$


$$\Sigma P = 208.3 \text{ mW}$$

$$4) I_{\text{source}} = I_{AB} + I_{AC} = 9.33 \text{ mA} + 11.53 \text{ mA} = \boxed{20.86 \text{ mA}}$$

$$P_{\text{source}} = 10 \text{ V} \times 0.02086 \text{ A} = \boxed{208.6 \text{ mW}}$$

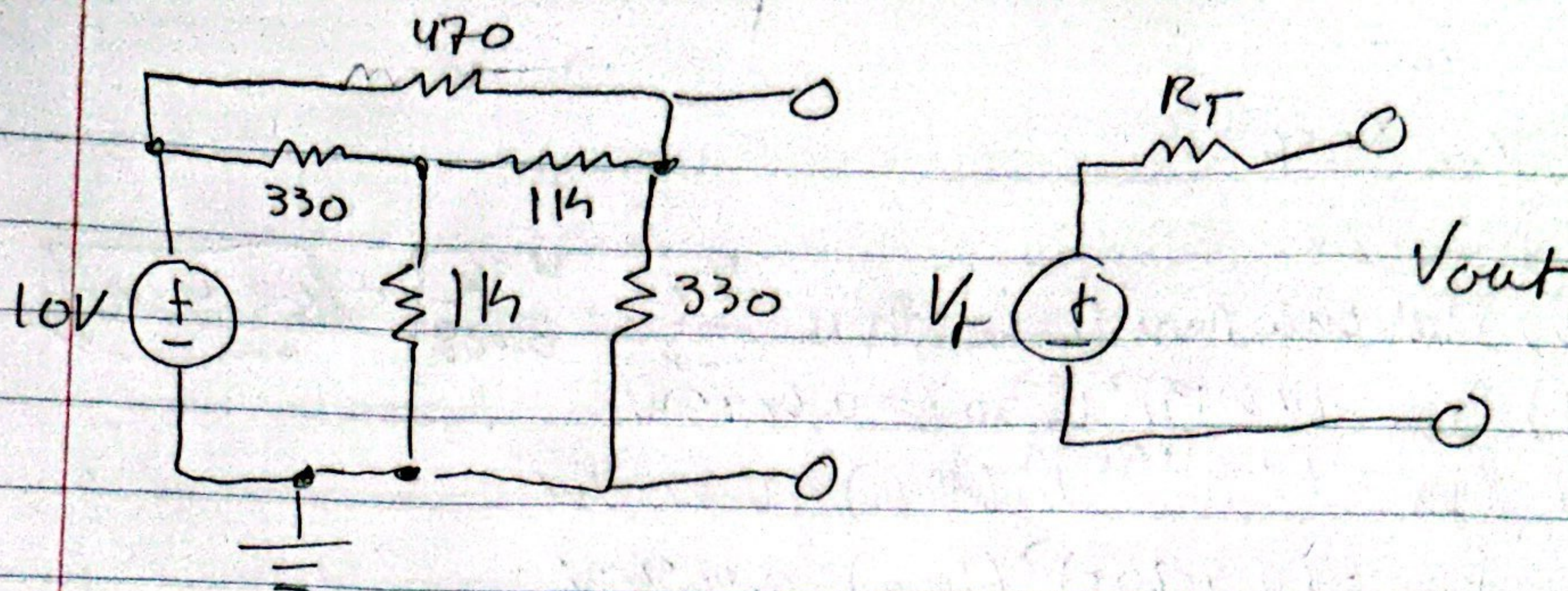5) error calculation (done in the lab)

Circuits Lab 1 Part 4 Thevenin equivalent circuits



• ground (bottom rail) = 0V

• node A = top of the source $\rightarrow V_A = 10V$

• node B = middle junction (330Ω , $1k\Omega$, $1k\Omega \downarrow$)

• node C = right terminal (joins 470Ω from A, $1k\Omega$ from B, 330Ω)
 $\rightarrow V_{out}$

Resistors: A-B: 330Ω ; B-C: $1k\Omega$, A-C: 470Ω , B-G: $1k\Omega$, C-G: 330Ω

open circuit voltage V_{oc} (V_{th})

1) Kcl at B-C

$$\text{node B: } \frac{V_B - 10}{330} + \frac{V_B - V_C}{1000} + \frac{V_B}{1000} = 0 \quad \boxed{V_B = 6.934V}$$

$$\text{node C: } \frac{V_C - 10}{470} + \frac{V_C - V_B}{1000} + \frac{V_C}{330} = 0 \quad \boxed{V_C = 4.581V}$$

$V_{oc} = V_{th} = 4.5183V$

2) Short circuit current I_{sc}

$$\frac{V_B - 10}{330} + \frac{V_B}{1000} + \frac{V_B}{1000} = 0 \quad \boxed{V_B = 6.024096V}$$

$$I_{sc} = \frac{10 - 0}{470} + \frac{V_B - 0}{1000} = 0.0212766 + 0.0060241 = 0.0273007A = 27mA$$

3) Thevenin resistance $R_{th} = \frac{V_{oc}}{I_{sc}} = \frac{4.581293}{0.0273007} = \boxed{167.809\Omega}$

1. 330Ω (C-G) 2. 470Ω (C-A=G)

3. $1k\Omega$ ($330\Omega \parallel 1000$) $R_3 = 1000 + (330 \parallel 1000) = 1000 + 248.12 = \boxed{1248.12\Omega}$

$$R_{eq} = \left(\frac{1}{330} + \frac{1}{470} + \frac{1}{1248} \right)^{-1} = \boxed{167.809\Omega}$$

$$\text{Verify } I = V_{th}/R_{th} = 4.518/167.809 = 27mA$$

Circuits
Lab 1

Part 4 actual

1) $V_{oc} = 4.56$

2) $I_x = 2.8$

3) Thevenin Resistance: $R_{TN} = \frac{V_{oc}}{I_x} = \frac{4.56}{0.028} = \underline{163.4 \Omega}$

4) $P_{gm} = (0.0093)^2 (330) = 0.0285 W$

$P_{g1} = (0.01157)^2 (470) = 0.0629 W$

$P_{m1} = (0.00237)^2 (1000) = 0.0056 W$

$P_{m2} = (0.00693)^2 (1000) = 0.0480 W$

$P_{R6} = (0.01382)^2 (330) = 0.0630 W$

$P_{total} = 0.208 W$

$I_2 = I_{gm} + I_{g1} = \underline{20.87 mA}$

5) Power $V_2 \cdot I_2 = (0.6)(0.02087) = \underline{0.0125 W}$

a very small difference can be seen.

Targeted because this circuit is following the
law of the conservation of energy